

Keywords: margining capability, dc-dc converters, D/A converters, DACs, current-output DACs

APPLICATION NOTE 4498

Add Margining Capability to a DC/DC Converter

By: Brian Vasquez

Nov 03, 2010

Abstract: You can easily add margining capability (digital adjustment of the output voltage) to a DC/DC converter by adding a 2- or 4-channel, I²C-adjustable current DAC (DS4402 or DS4404) at the converter's feedback input. Because each DAC output is 0mA at power up, the extra circuitry is transparent to the system until a command is written via the I²C bus.

A similar version of this article appeared in the September 18, 2008 issue of *EDN* magazine.

You can easily add margining capability to a DC/DC converter (digital adjustment of the output voltage) by making a single connection to the existing circuit as shown by the dotted line in **Figure 1**. The extra IC is a 2- or 4-channel, I²C-adjustable current DAC (DS4402 or DS4404). Because each DAC output is 0mA at power up, the extra circuitry is essentially transparent to the system until a command is written via the I²C bus.

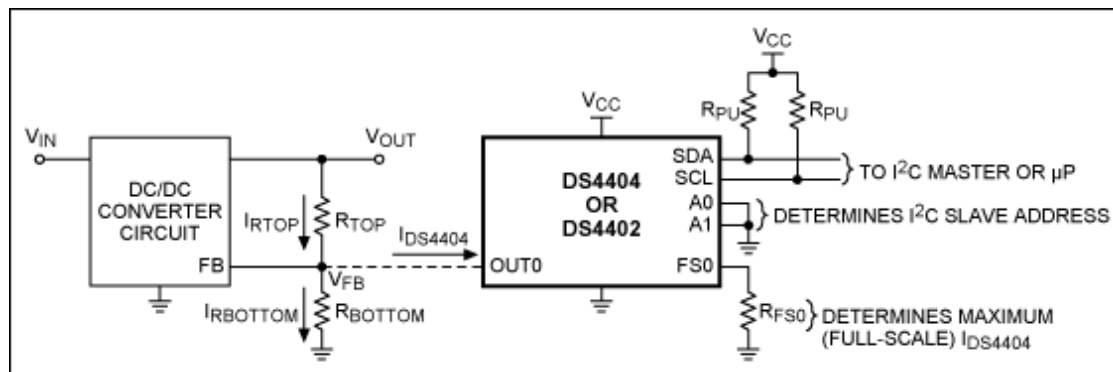


Figure 1. Circuitry on the right, added to the feedback input of a DC/DC converter, adds margining capability to the converter.

As an example, assume $V_{IN} = 3V$ to $5.5V$, $V_{OUT} = 1.8V$ (the desired nominal output voltage), and $V_{FB} = 0.6V$ (not to be confused with V_{REF} of the DS4404). You can obtain the V_{FB} value from the DC/DC converter datasheet, being sure to verify that it is within the OUTx voltage range specified in the current DAC datasheet (specified as $V_{OUT:SINK}$ and $V_{OUT:SOURCE}$ depending on whether you are sinking or sourcing current). It's also important to verify the input impedance of the DC/DC converter's FB pin (the circuit shown assumes a high impedance).

Assume we want to add a $\pm 20\%$ margining capability to the DC/DC converter output (V_{OUT}):

$$V_{OUTMAX} = 2.16V$$

$$V_{OUTNOM} = 1.8V$$

$$V_{OUTMIN} = 1.44V$$

First, determine the necessary relationship between R_{TOP} and R_{BOTTOM} that yields the nominal output (V_{OUTNOM}) when $I_{DS4404} = 0A$:

$$V_{FB} = V_{OUTNOM} \left(\frac{R_{BOTTOM}}{R_{BOTTOM} + R_{TOP}} \right)$$

Solving for R_{TOP} ,

$$R_{TOP} = R_{BOTTOM} \left(\frac{V_{OUTNOM}}{V_{FB}} - 1 \right) \quad (\text{Eq. 1})$$

For our example,

$$R_{TOP} = R_{BOTTOM} \left(\frac{1.8V}{0.6V} - 1 \right) = 2 \times R_{BOTTOM}$$

The current (I_{DS4404}) required to make V_{OUT} increase to V_{OUTMAX} is derived by summing currents at the FB node:

$$I_{RTOP} = I_{RBOTTOM} + I_{DS4404}$$

$$I_{DS4404} = I_{RTOP} - I_{RBOTTOM}$$

$$I_{RTOP} = \left(\frac{V_{OUTMAX} - V_{FB}}{R_{TOP}} \right), I_{RBOTTOM} = \left(\frac{V_{FB}}{R_{BOTTOM}} \right) \quad (\text{Eq. 2})$$

$$I_{DS4404} = \left(\frac{V_{OUTMAX} - V_{FB}}{R_{TOP}} \right) - \left(\frac{V_{FB}}{R_{BOTTOM}} \right)$$

This equation can be simplified by solving Equation 1 for R_{BOTTOM} and substituting, which yields:

$$I_{DS4404} = \frac{V_{OUTMAX} - V_{OUTNOM}}{R_{TOP}}$$

In terms of margin percentage:

$$I_{DS4404} = \frac{V_{OUTMAX} \times \text{MARGIN}}{R_{TOP}} \quad (\text{Eq. 3})$$

where margin = 0.2, to implement $\pm 20\%$ margining in this case. Before you can use this relationship to calculate R_{TOP} and R_{BOTTOM} , you must select the full-scale current I_{FS} .

According to the DS4404 datasheet, the full-scale current (specified as $I_{OUT:SINK}$ or $I_{OUT:SOURCE}$) must be between 0.5mA and 2.0mA, to guarantee the specifications for accuracy and linearity. Unfortunately, no formula is available for calculating the ideal full-scale current. That value is influenced by the desired number of steps, the step size, and the values for R_{TOP} and R_{BOTTOM} . Another factor affecting the full-scale current value would be the requirement that a particular register setting correspond to a particular margin percentage.

In any case, your selection of a full-scale current will likely require several iterations, in which you select an arbitrary value (within the range), and then calculate R_{TOP} , R_{BOTTOM} , R_{FS} , and step size. When you've determined an acceptable full-scale current value, you may want to further adjust it (or some of the

resistor values) to ensure that the resistor values finally specified are commonly available.

To calculate R_{TOP} for the original example, we choose $I_{FS} = I_{DS4404}$, which gives us 31 equal increments (steps) from V_{OUTNOM} to V_{OUTMAX} , as well as 31 steps from V_{OUTNOM} to V_{OUTMIN} . This resolution is more than adequate for our example. We could, for instance, begin by arbitrarily choosing I_{FS} in the center (1.25mA) of the specified range, and then performing all the calculations. Instead, for illustrative purposes we perform calculations for the endpoints of the range (0.5mA, 2.0mA).

So, for $I_{FS} = I_{DS4404} = 0.5\text{mA}$: Using Equation 3 and solving for R_{TOP} ,

$$R_{TOP} = \frac{V_{OUTNOM} \times \text{MARGIN}}{I_{DS4404}} = \frac{1.8 \times 0.2}{0.5 \times 10^{-3}} = 720\Omega$$
$$R_{BOTTOM} = \frac{R_{TOP}}{2} = \frac{720}{2} = 360\Omega$$

To calculate R_{FS} , use the formula in the DS4404 datasheet plus the V_{REF} value also found in that datasheet:

$$R_{FS} = \frac{V_{REF}}{I_{FS}} \times \frac{31}{4} = \frac{1.23}{0.5 \times 10^{-3}} \times \frac{31}{4} = 19,065\Omega = 19\text{k}\Omega$$
$$\text{STEP SIZE} = \frac{I_{FS}}{\text{NUMBER OF STEPS}} = \frac{0.5 \times 10^{-3}}{31} = 16.1\mu\text{A/STEP}$$

Finally, for completeness we determine the DS4404 output current as a function of register setting:
 $I_{OUT}(\text{register setting}) = \text{step size} \times \text{register setting}$.

Note that the register setting above does not include the sign bit, which is used to select sink or source. The DS4404 sinks current when the sign bit = 0, making V_{OUT} increase to V_{OUTMAX} . It sources current when the sign bit = 1, making V_{OUT} decrease towards V_{OUTMIN} .

For $I_{FS} = I_{DS4404} = 2.0\text{mA}$:

$$R_{TOP} = \frac{V_{OUTNOM} \times \text{MARGIN}}{I_{DS4404}} = \frac{1.8 \times 0.2}{2.0 \times 10^{-3}} = 180\Omega$$
$$R_{BOTTOM} = \frac{R_{TOP}}{2} = \frac{180}{2} = 90\Omega$$
$$R_{FS} = \frac{V_{REF}}{I_{FS}} \times \frac{31}{4} = \frac{1.23}{2.0 \times 10^{-3}} \times \frac{31}{4} = 4,766\Omega = 4.7\text{k}\Omega$$
$$\text{STEP SIZE} = \frac{I_{FS}}{\text{NUMBER OF STEPS}} = \frac{2.0 \times 10^{-3}}{31} = 64.5\mu\text{A/STEP}$$

Comparing R_{TOP} and R_{BOTTOM} for the two cases ($I_{FS} = 0.5\text{mA}$ vs. 2.0mA), you can see that $I_{FS} = 0.5\text{mA}$ is more attractive because the resistances are higher.

Related Parts

[DS4404](#) Two/Four-Channel, I²C Adjustable Current DAC

[Free Samples](#)

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>
Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 4498: <http://www.maximintegrated.com/an4498>
APPLICATION NOTE 4498, AN4498, AN 4498, APP4498, Appnote4498, Appnote 4498
Copyright © by Maxim Integrated Products
Additional Legal Notices: <http://www.maximintegrated.com/legal>